
Karnaugh Maps (K-Maps)

- A visual way to simplify logic expressions
- It gives the most simplified form of the expression

Rules to obtain the most simplified expression

- Simplification of logic expression using Boolean algebra is awkward because:
 - it lacks specific rules to predict the most suitable next step in the simplification process
 - it is difficult to determine whether the simplest form has been achieved.
- A Karnaugh map is a graphical method used to obtain the most simplified form of an expression in a standard form (Sum-of-Products or Product-of-Sums).
- The simplest form of an expression is the one that has the minimum number of terms with the least number of literals (variables) in each term.
- By simplifying an expression to the one that uses the minimum number of terms, we ensure that the function will be implemented with the minimum number of gates.
- By simplifying an expression to the one that uses the least number of literals for each term, we ensure that the function will be implemented with gates that have the minimum number of inputs.

Three-Variable K-Maps

$$f = \sum(0,4) = \bar{B}\bar{C}$$

		BC			
		00	01	11	10
A	0	1	0	0	0
	1	1	0	0	0

$$f = \sum(4,5) = A\bar{B}$$

		BC			
		00	01	11	10
A	0	0	0	0	0
	1	1	1	0	0

$$f = \sum(0,1,4,5) = \bar{B}$$

		BC			
		00	01	11	10
A	0	1	1	0	0
	1	1	1	0	0

$$f = \sum(0,1,2,3) = \bar{A}$$

		BC			
		00	01	11	10
A	0	1	1	1	1
	1	0	0	0	0

$$f = \sum(0,4) = \bar{A}C$$

		BC			
		00	01	11	10
A	0	0	1	1	0
	1	0	0	0	0

$$f = \sum(4,6) = A\bar{C}$$

		BC			
		00	01	11	10
A	0	0	0	0	0
	1	1	0	0	1

$$f = \sum(0,2) = \bar{A}\bar{C}$$

		BC			
		00	01	11	10
A	0	1	0	0	1
	1	0	0	0	0

$$f = \sum(0,2,4,6) = \bar{C}$$

		BC			
		00	01	11	10
A	0	1	0	0	1
	1	1	0	0	1

Three-Variable K-Map Examples

A \ BC	00	01	11	10
0		1		
1	1		1	1

A \ BC	00	01	11	10
0	1		1	1
1	1			1

A \ BC	00	01	11	10
0			1	1
1	1	1		

A \ BC	00	01	11	10
0			1	
1	1		1	1

A \ BC	00	01	11	10
0		1	1	1
1		1	1	

A \ BC	00	01	11	10
0				
1				

Four-Variable K-Maps

		CD			
	AB	00	01	11	10
00		1	0	0	0
01		0	0	0	0
11		0	0	0	0
10		1	0	0	0

$$f = \sum(0,8) = \bar{B} \cdot \bar{C} \cdot \bar{D}$$

		CD			
	AB	00	01	11	10
00		0	0	0	0
01		0	1	0	0
11		0	1	0	0
10		0	0	0	0

$$f = \sum(5,13) = B \cdot \bar{C} \cdot D$$

		CD			
	AB	00	01	11	10
00		0	0	0	0
01		0	0	0	0
11		0	1	1	0
10		0	0	0	0

$$f = \sum(13,15) = A \cdot B \cdot D$$

		CD			
	AB	00	01	11	10
00		0	0	0	0
01		1	0	0	1
11		0	0	0	0
10		0	0	0	0

$$f = \sum(4,6) = \bar{A} \cdot B \cdot \bar{D}$$

		CD			
	AB	00	01	11	10
00		0	0	1	1
01		0	0	1	1
11		0	0	0	0
10		0	0	0	0

$$f = \sum(2,3,6,7) = \bar{A} \cdot C$$

		CD			
	AB	00	01	11	10
00		0	0	0	0
01		1	0	0	1
11		1	0	0	1
10		0	0	0	0

$$f = \sum(4,6,12,14) = B \cdot \bar{D}$$

		CD			
	AB	00	01	11	10
00		0	0	1	1
01		0	0	0	0
11		0	0	0	0
10		0	0	1	1

$$f = \sum(2,3,10,11) = \bar{B} \cdot C$$

		CD			
	AB	00	01	11	10
00		1	0	0	1
01		0	0	0	0
11		0	0	0	0
10		1	0	0	1

$$f = \sum(0,2,8,10) = \bar{B} \cdot \bar{D}$$

Four-Variable K-Maps

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	1	1	1	1
	11	0	0	0	0
	10	0	0	0	0

$$f = \sum(4,5,6,7) = \bar{A} \bullet B$$

		CD			
		00	01	11	10
AB	00	0	0	1	0
	01	0	0	1	0
	11	0	0	1	0
	10	0	0	1	0

$$f = \sum(3,7,11,15) = C \bullet D$$

		CD			
		00	01	11	10
AB	00	1	0	1	0
	01	0	1	0	1
	11	1	0	1	0
	10	0	1	0	1

$$f = \sum(0,3,5,6,9,10,12,15)$$

$$f = A \otimes B \otimes C \otimes D$$

		CD			
		00	01	11	10
AB	00	0	1	0	1
	01	1	0	1	0
	11	0	1	0	1
	10	1	0	1	0

$$f = \sum(1,2,4,7,8,11,13,14)$$

$$f = A \oplus B \oplus C \oplus D$$

		CD			
		00	01	11	10
AB	00	0	1	1	0
	01	0	1	1	0
	11	0	1	1	0
	10	0	1	1	0

$$f = \sum(1,3,5,7,9,11,13,15)$$

$$f = D$$

		CD			
		00	01	11	10
AB	00	1	0	0	1
	01	1	0	0	1
	11	1	0	0	1
	10	1	0	0	1

$$f = \sum(0,2,4,6,8,10,12,14)$$

$$f = \bar{D}$$

		CD			
		00	01	11	10
AB	00	0	0	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	0	0	0	0

$$f = \sum(4,5,6,7,12,13,14,15)$$

$$f = B$$

		CD			
		00	01	11	10
AB	00	1	1	1	1
	01	0	0	0	0
	11	0	0	0	0
	10	1	1	1	1

$$f = \sum(0,1,2,3,8,9,10,11)$$

$$f = \bar{B}$$

Four-Variable K-Maps Examples

AB \ CD	CD			
	00	01	11	10
00	1	1		1
01	1	1		1
11	1	1		1
10	1	1		

AB \ CD	CD			
	00	01	11	10
00	1	1		1
01				1
11				
10	1	1		1

AB \ CD	CD			
	00	01	11	10
00				
01	1	1	1	
11	1	1		1
10	1			

AB \ CD	CD			
	00	01	11	10
00		1	1	
01	1	1	1	1
11	1		1	1
10			1	

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

Four-Variable K-Maps Examples

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

Four-Variable K-Maps Examples

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

Design of combinational digital circuits

- Steps to design a combinational digital circuit:
 - From the problem statement derive the truth table
 - From the truth table derive the unsimplified logic expression
 - Simplify the logic expression
 - From the simplified expression draw the logic circuit
- Example: Design a 3-input (A,B,C) digital circuit that will give at its output (X) a logic 1 only if the binary number formed at the input has more ones than zeros.

	Inputs			Output
	A	B	C	X
0	0	0	0	0
1	0	0	1	0
2	0	1	0	0
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	1
7	1	1	1	1


→ $X = \sum (3, 5, 6, 7)$

↓

A	BC			
	00	01	11	10
0	0	0	1	0
1	0	1	1	1

↓

$$X = AC + AB + BC$$

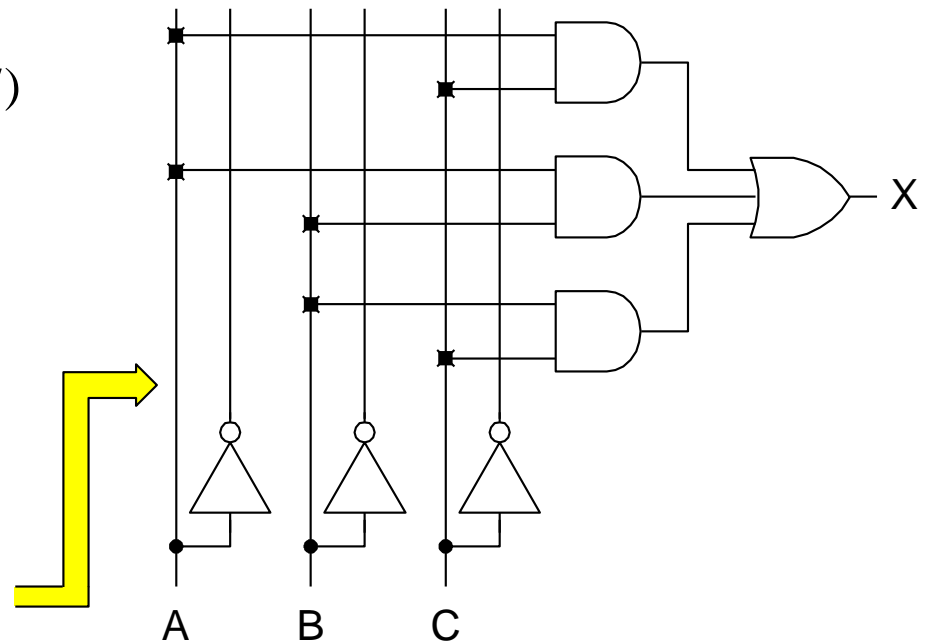

Design of combinational digital circuits (Cont.)

- Example: Design a 4-input (A,B,C,D) digital circuit that will give at its output (X) a logic 1 only if the binary number formed at the input is between 2 and 9 (including).

	Inputs				Output X
	A	B	C	D	
0	0	0	0	0	0
1	0	0	0	1	0
2	0	0	1	0	1
3	0	0	1	1	1
4	0	1	0	0	1
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	1
8	1	0	0	0	1
9	1	0	0	1	1
10	1	0	1	0	0
11	1	0	1	1	0
12	1	1	0	0	0
13	1	1	0	1	0
14	1	1	1	0	0
15	1	1	1	1	0


→ $X = \sum (2,3,4,5,6,7,8,9)$

↓

CD		AB			
		00	01	11	10
00	00	0	0	1	1
	01	1	1	1	1
11	00	0	0	0	0
	01	1	1	0	0

↓
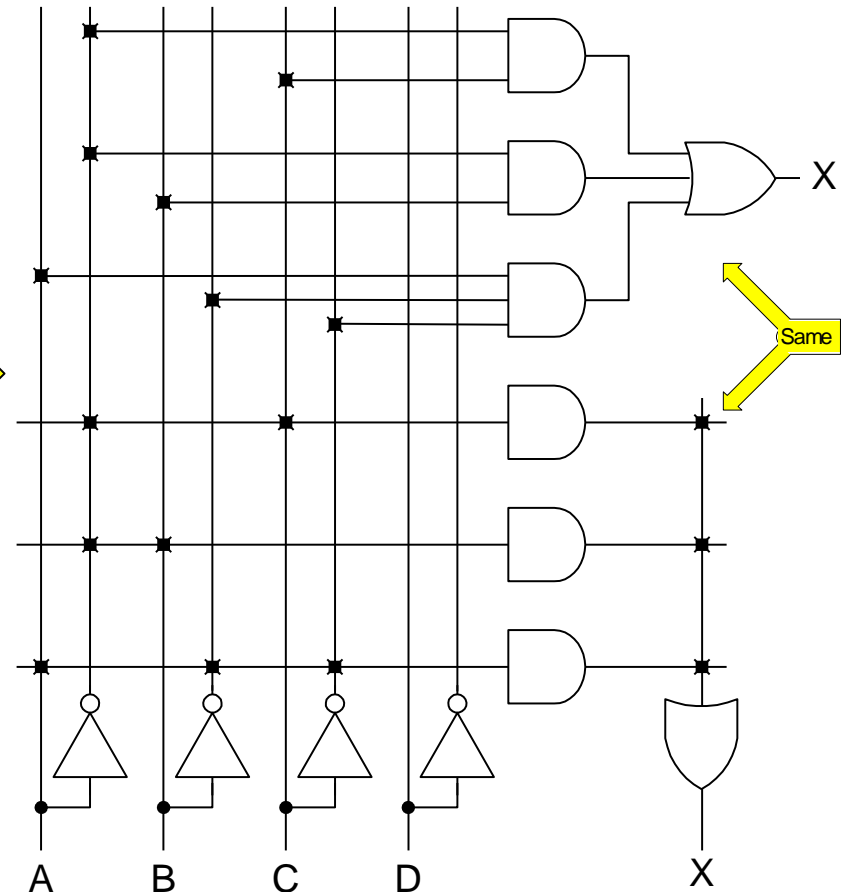
$$X = \bar{A}C + \bar{A}B + A\bar{B}\bar{C}$$



Design of combinational digital circuits (Example)

- Example: Design a 4-input (A,B,C,D) digital circuit that will give at its output (X) a logic 1 only if there more ones than zeros in the binary number formed at the input.

	Inputs				Output	
	A	B	C	D		
0	0	0	0	0		
1	0	0	0	1		
2	0	0	1	0		
3	0	0	1	1		
4	0	1	0	0		
5	0	1	0	1		
6	0	1	1	0		
7	0	1	1	1		
8	1	0	0	0		
9	1	0	0	1		
10	1	0	1	0		
11	1	0	1	1		
12	1	1	0	0		
13	1	1	0	1		
14	1	1	1	0		
15	1	1	1	1		

X =

AB \ CD	CD			
	00	01	11	10
00				
01				
11				
10				

X =

