

LOGIC GATES

**PRESENTED BY:
DR. VIVEK AMBALKAR
HOD, PHYSICS
D. P. VIPRA COLLEGE**

WHAT IS

2

GATE

A device that performs a basic operation on electrical signals

CIRCUITS

Gates combined to perform more complicated tasks

How do we describe the behavior of gates and circuits?

3

Boolean expressions

Uses Boolean algebra, a mathematical notation for expressing two-valued logic

Logic diagrams

A graphical representation of a circuit; each gate has its own symbol

Truth tables

A table showing all possible input value and the associated output values

Gates

4

Six types of gates

- NOT
- AND
- OR
- XOR
- NAND
- NOR

Typically, logic diagrams are black and white with gates distinguished only by their shape

We use color for emphasis (and fun)

NOT Gate


5

A NOT gate accepts one input signal (0 or 1) and returns the opposite signal as output

Boolean Expression

$$X = A'$$

Logic Diagram Symbol

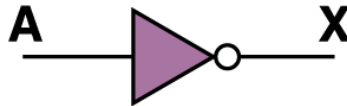

Truth Table

A	X
0	1
1	0

Figure 1 Various representations of a NOT gate

AND Gate


6

An AND gate accepts two input signals
If both are 1, the output is 1; otherwise,
the output is 0

Boolean Expression

$$X = A \cdot B$$

Logic Diagram Symbol

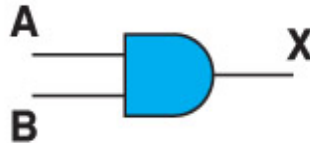

Truth Table

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

Figure 2 Various representations of an AND gate

OR Gate

7

An OR gate accepts two input signals

If both are 0, the output is 0; otherwise, the output is 1

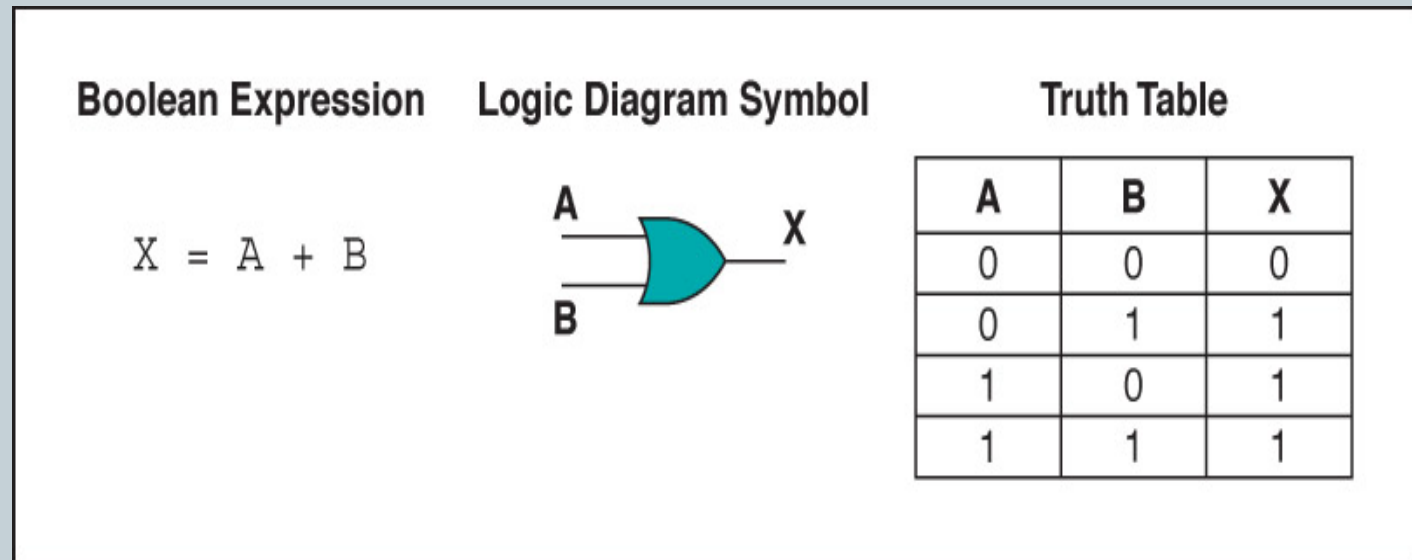


Figure 3 Various representations of a OR gate

XOR Gate

8

An XOR gate accepts two input signals

If both are the same, the output is 0; otherwise, the output is 1

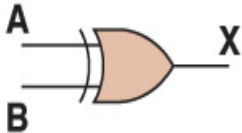
Boolean Expression	Logic Diagram Symbol	Truth Table															
$X = A \oplus B$		<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0
A	B	X															
0	0	0															
0	1	1															
1	0	1															
1	1	0															

Figure 4 Various representations of an XOR gate

XOR Gate

9

Note the difference between the **XOR** gate and the **OR** gate; they differ only in one input situation

When both input signals are 1, the OR gate produces 1 and the XOR produces 0

XOR is called the *exclusive OR*

NAND Gate




The NAND gate accepts two input signals
If both are 1, the output is 0; otherwise,
the output is 1

Boolean Expression

$$X = (A \cdot B)'$$

Logic Diagram Symbol

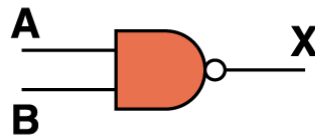

Truth Table

A	B	X
0	0	1
0	1	1
1	0	1
1	1	0

Figure 5 Various representations of a NAND gate

NOR Gate

11

The NOR gate accepts two input signals
If both are 0, the output is 1; otherwise,
the output is 0

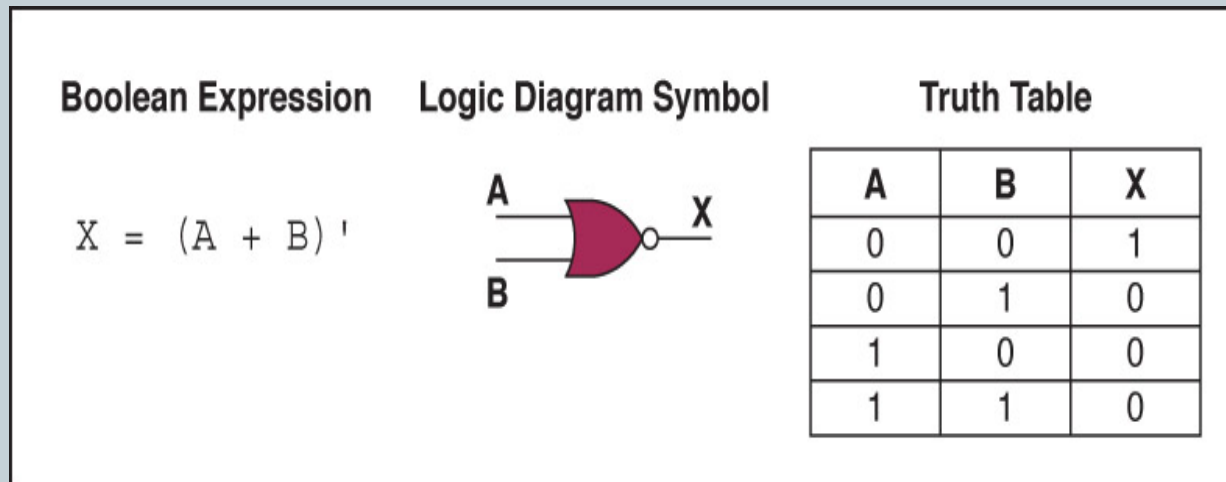


Figure 6 Various representations of a NOR gate

Review of Gate Processing

12

A **NOT** gate **inverts** its single input

An **AND** gate produces **1** if **both** input values are **1**

An **OR** gate produces **0** if **both** input values are **0**

An **XOR** gate produces **0** if input values are the **same**

A **NAND** gate produces **0** if **both** inputs are **1**

A **NOR** gate produces a **1** if both inputs are **0**

THANK YOU